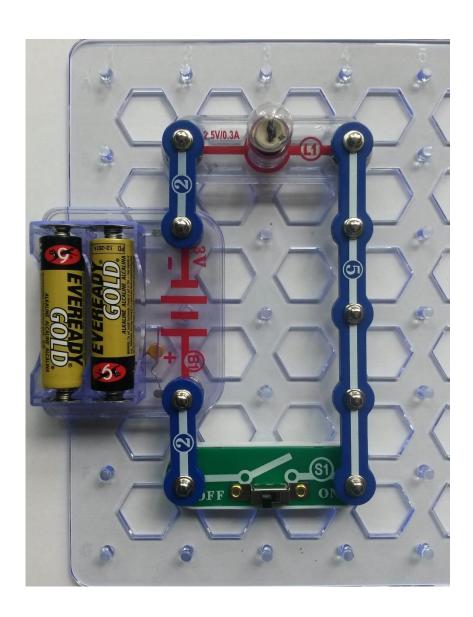
Single Bulb (with switch) Circuit Picture



Key:

Light Bulb

Battery OR — | +

Switch ——O

Circuit diagram for a single light bulb and switch:

